



DEPARTMENT OF ELECTRONICS AND
ELECTRICAL COMMUNICATION
ENGINEERING, IIT KHARAGPUR

Experiment 2: Switching Modulator


Samyak Sheersh, Souhardya Bose, Aryam Shankar

Roll Numbers: 22EC30045, 21EE10097, 22EC3FP37
Group Number: 12

06 August 2024

1 Introduction

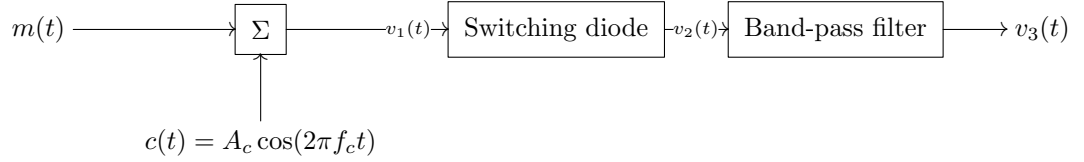We want to transmit a message signal $m(t)$ using a carrier signal $c(t)$. We set up the following to generate the final modulated signal, and the following block diagram represents it:



Here

$$v_1(t) = m(t) + A_c \cos(2\pi f_c t)$$

where $A_c > |m(t)|$

Due to the diode:

$$v_2(t) = \begin{cases} v_1(t), & \text{if } c(t) > 0 \\ 0, & \text{if } c(t) < 0 \end{cases} \quad (1)$$

which means that the expression can be represented as:

$$v_2(t) = v_1(t)x(t) \quad (2)$$

where $x(t)$ is a square wave which follows $\cos(2\pi f_c t)$

The Fourier decomposition can be written as

$$x(t) = \frac{1}{2} + \frac{2}{\pi} \sum_{n=1}^{\infty} \left(\frac{(-1)^{n-1}}{2n-1} \cos(2\pi(2n-1)f_c t) \right) \quad (3)$$