



DEPARTMENT OF ELECTRONICS AND
ELECTRICAL COMMUNICATION
ENGINEERING, IIT KHARAGPUR

Experiment 6: Sampling

Samyak Sheersh, Souhardya Bose, Aryam Shankar

Roll Numbers: 22EC30045, 21EE10097, 22EC3FP37
Group Number: 12

21 October 2024

1 Introduction

1.1 Objectives

1. To sample and hold a given input signal
2. To generate a Pulse Amplitude Modulated(PAM) signal

2 Instruments and Materials Used

1. RIGOL Signal Generator
2. ScientiFIC SMO10C Digital Signal Oscilloscope
3. +12V, -12V DC source and ground
4. Resistors
5. Capacitors
6. Diodes
7. Breadboard
8. Connecting wires
9. JFET
10. Potentiometer

3 Theory

A sample and hold circuit is frequently used in analog-to-digital conversion system, and it holds the value for a certain period allowing further processing to happen, and is essential to digitize and store signals. In relation to this circuit, we define two terms:

1. Aperture time: The time during which the sampling occurs. Ideally we want it to be zero i.e store instantaneous precise values, but we strive to keep it as short as possible.
2. Hold time: The duration in which the sampled value is held constant by the capacitor.

A Pulse Amplitude Modulation(PAM) is a form of signal modulation where the amplitude of a series of pulses is varied according to the instantaneous values of the signal

4 Circuit Diagram

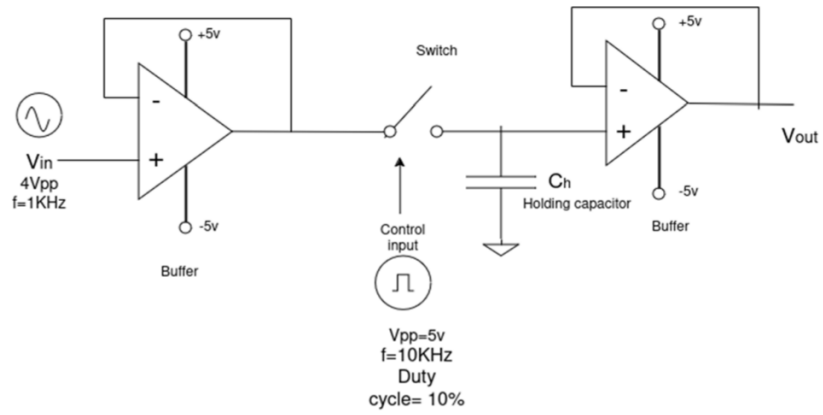


Figure 1: A sample and hold circuit diagram

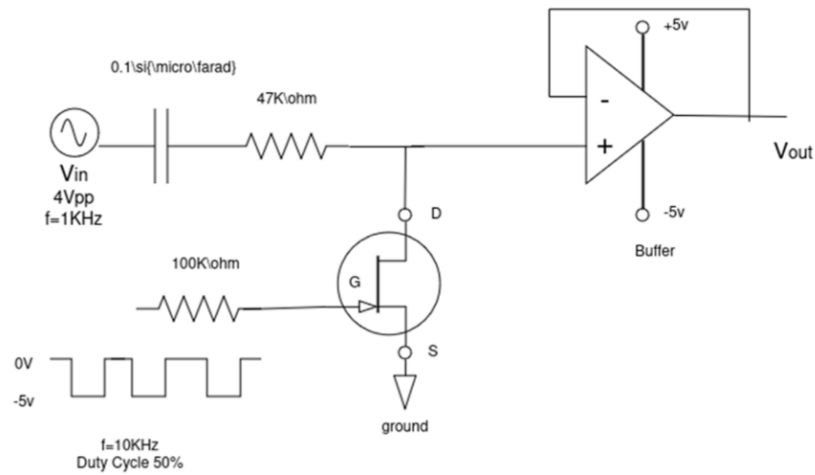


Figure 2: PAM Circuit diagram

5 Calculations

We have the frequency of the pulse as $f_s = 10kHz$ and the frequency of the message signal is $f_m = 1kHz$

5.1 Task 1

We want the capacitor to be about 99% full i.e. the sampled value should be about 99% of the maximum value achievable. Thus we need to choose a capacitor, such that the time constant for the resulting circuit is small enough that it gets filled fast enough before we need to discharge and record the next sample.

Let $\tau = R_{ON}C$ be the time constant where R_{ON} is the resistance of the JFET when it is switched on by the pulse on the gate. Let the period of the pulse be T and D be the duty cycle(expressed in percentage). We know that it takes 5τ for an RC circuit to achieve 99% of the maximum charge achievable on the capacitor. Since the signal is only going to remain in ON state for time DT , we need to ensure that:

$$5\tau < DT \quad (1)$$

$$\Rightarrow C < \frac{DT}{5R_{ON}} \quad (2)$$

We found $R_{ON} = 300k\Omega$ from the datasheet, and the time period of the pulse is $T = \frac{1}{f_s} = 10^{-4}s$ and the duty cycle is $D = 10\%$. Thus the capacitor should be $C < 660pF$. We took the capacitor with $C = 220pF$

We also added a DC offset of +3V since a negative voltage across the JFET led to distortions in the final signal. By adding the offset, we ensured that there was no negative voltage across the drain and the source of the JFET.

5.2 Task 2

We were specified that the pulse varied from 0 to -5V, So we sent a pulse with $V_{pp} = 5V$ and an offset of -2.5V. Since a negative V_{GS} leads to an increased depletion layer, the negative voltage causes the JFET to behave like an open and closed circuit during the ON and OFF time respectively. This time the duty cycle was $D = 50\%$.

We used a message signal with $V_{pp} = 5V$ with no offset in this case.

6.1 Task 1

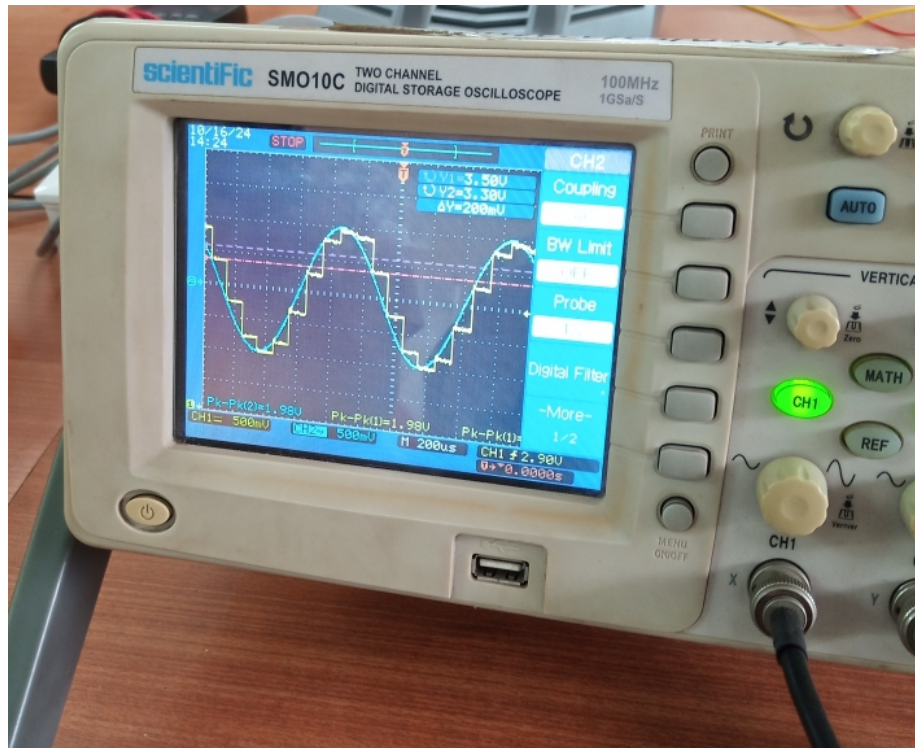


Figure 3: Sample and hold with duty cycle=10%

 


Figure 4: Sample and hold with duty cycle=50%

 


Figure 5: Sample and hold with duty cycle=80%

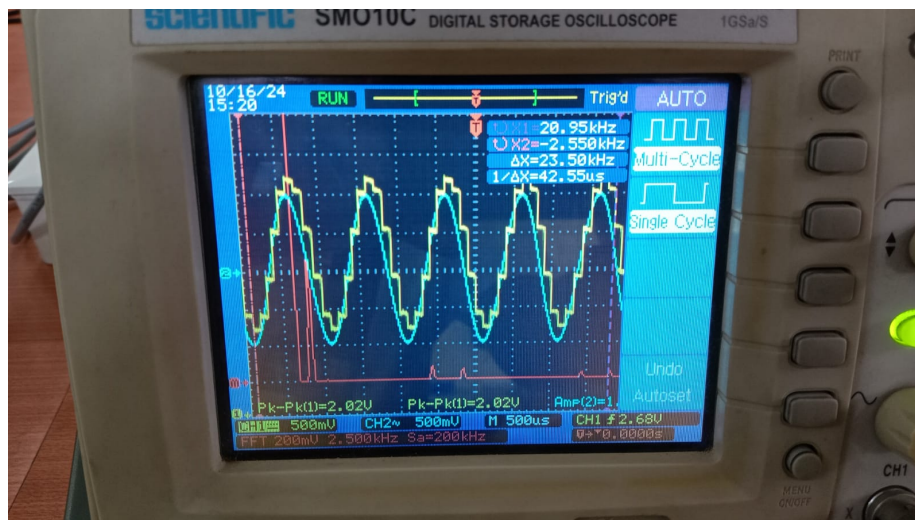


Figure 6: FFT of the sample and hold signal for $D=10\%$

6.2 Task 2

 


Figure 7: Pulse Amplitude Modulated signal with duty cycle=50%

 


Figure 8: FFT of the PAM signal for D=50%

7 Discussion

7.1 Samyak Sheersh, 22EC30045

1. As we increased the duty cycle in task 1, we saw the sample and hold converging on to the signal $m(t)$ see Figures 3, 4 and 5. this is expected since a longer duty cycle essentially means that the signal has time to evolve within the aperture time and in the limiting case of $D = 100\%$, the circuit just becomes an all pass filter and the output is just the signal $m(t)$
2. We found that for the sample and hold signal(i.e Task 1 with $D = 10\%$), there were peaks in the FFT at $n \cdot f_s \pm f_m = 10n \pm 1$ kHz for $\forall n \in \mathbb{N}$ except for a peak at the original $f_m = 1kHz$ and a peak at $f = 0$ because of the DC offset.
3. We found that for the PAM signal(i.e Task 2), there were peaks in the FFT at $(2n - 1) \cdot f_s \pm f_m = 10(2n - 1) \pm 1$ kHz for $\forall n \in \mathbb{N}$ except for a peak at the original $f_m = 1kHz$.
4. This difference in the frequencies present in both the signals is also expected since, for the duty cycle at 50% for Task 2, the pulse becomes a square wave which we know has only odd harmonics, while the pulse with just 10% duty cycle behaves much more like an impulse and its Fourier transform is a *sinc* function i.e the magnitude of the coefficients decays but is non zero for all harmonics, even or odd.
5. We also had to add an offset to the signal in Task 1, since a negative V_{DS} was causing distortion in the final signal, which may occur because the reverse flow of current from Source to drain may not be linear in nature and the resulting voltage that we measure may get affected.
6. We saw a tradeoff on varying the capacitance. A smaller capacitance would charge up quickly, but it would also discharge quickly and since the total charge on it is less, the voltage reading was also a bit noisy. While larger capacitor took a longer time to charge and discharge, they were less noisy, thus we selected $C = 220pF$ instead of something like $20pF$.